 


Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - Flip-Flop D




```
library ieee;
use ieee.std_logic_1164.all;

entity ffd is
    port (ck, clr, set, d : in  std_logic;
          q : out std_logic);
end ffd;

architecture logica of ffd is
begin
    process(ck, clr, set)
    begin
        if      (set = '0')           then q <= '1';
        elsif  (clr = '0')           then q <= '0';
        elsif  (ck'event and ck = '1') then q <= d;
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - Registrador de 3 bits com entradas síncronas




```
library ieee;
use ieee.std_logic_1164.all;

entity reg3bs is
    port (ck, clr, set : in  std_logic;
          d : in  std_logic_vector(2 downto 0);
          q : out std_logic_vector(2 downto 0));
end reg3bs;

architecture logica of reg3bs is
begin
    process (ck)
    begin
        if (ck'event and ck = '1') then
            if (clr = '1') then q <= "000"; -- condicao do sinal relógio
            elsif (set = '1') then q <= "111"; -- teste para levar q=000
            else q <= d; -- teste para levar q=111
            end if;
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - Registrador de 3 bits com entradas assíncronas




```
library ieee;
use ieee.std_logic_1164.all;

entity reg3ba is
    port (ck, clr, set : in  std_logic;
          d : in  std_logic_vector(2 downto 0);
          q : out std_logic_vector(2 downto 0));
end reg3ba;

architecture logica of reg3ba is
begin
    process (ck, clr, set)
    begin
        if      (clr = '1')           then q <="000"; -- q=000 independente de ck
        elsif  (set = '1')           then q <="111"; -- q=111 independente de ck
        elsif  (ck'event and ck = '1') then q <=d;    -- condicao do sinal relógio
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - Registrador de 3 bits com entradas assíncronas e habilitador




```
library ieee;
use ieee.std_logic_1164.all;

entity reg3ba_en is
    port (ck, clr, set, ld : in  std_logic;
          d : in  std_logic_vector(2 downto 0);
          q : out std_logic_vector(2 downto 0));
end reg3ba_en;

architecture logica of reg3ba_en is
begin
    process (ck, clr, set)
    begin
        if (clr = '1') then q <= "000";    -- q=000 independente de ck
        elsif (set = '1') then q <= "111"; -- q=111 independente de ck
        elsif (ck'event and ck = '1') then -- detecta borda de ck
            if (ld = '1') then q <= d;     -- verifica habilitacao
            end if;
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - MDE sequencial

 


```
use ieee.std_logic_1164.all;

entity mde is
    port (ck, rst : in std_logic;
          q       : out std_logic);
end mde;

architecture logica of mde is
begin
    process (ck, rst)
    begin
        if rst = '1' then                                -- estado inicial
            q <= "00";
        elsif (ck'event and ck = '1') then               -- ciclo de estados
            case q is
                when "00" => q <= "01";
                when "01" => q <= "11";
                when "11" => q <= "10";
                when "10" => q <= "00";
            end case;
        end if;
    end process;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - MDE do tipo Moore com um processo



```
use ieee.std_logic_1164.all;

entity mde is
    port (ck, rst, sobe : in std_logic;
          q : out std_logic);
end mde;


architecture logica of mde is
    type st is (caso_d, caso_c, caso_b, caso_a);
    signal estado : st;

begin
    process (ck, rst)
    begin
        if rst = '1' then
            estado <= caso_a;
        elsif (ck'event and ck = '1') then
            case estado is
                when caso_a =>
                    if sobe = '1' then estado <= caso_b;
                    else estado <= caso_d;
                    end if;
                when caso_b =>
                    if sobe = '1' then estado <= caso_c;
                    else estado <= caso_a;
                    end if;
                when caso_c =>
                    if sobe = '1' then estado <= caso_d;
                    else estado <= caso_b;
                    end if;
                when caso_d =>
                    if sobe = '1' then estado <= caso_a;
                    else estado <= caso_c;
                    end if;
            end case;
        end if;
    end process;

    with estado select
        q <= "00" when caso_a,
              "01" when caso_b,
              "11" when caso_c,
              "10" when caso_d;
end logica;
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

 Material de suporte - MDE do tipo Moore com dois processos



```

library ieee;
use ieee.std_logic_1164.all;

entity mde_b is
    port (ck, rst, w : in std_logic;
          z : out std_logic);
end mde_b;

architecture logica of mde_b is
    type state_type is (a, b, c);
    signal y_present, y_next : state_type;


begin
    process (w, y_present)
    begin
        case y_present is
            when a =>
                if w = '0' then y_next <= a;
                else y_next <= b; end if;
            when b =>
                if w = '0' then y_next <= a;
                else y_next <= c; end if;
            when c =>
                if w = '0' then y_next <= a;
                else y_next <= c; end if;
        end case;
    end process;

    process (ck, rst)
    begin
        if rst = '0' then
            y_present <= a;
        elsif (ck'event and ck = '1') then
            y_present <= y_next;
        end if;
    end process;

    z <= '1' when y_present = c else '0';
end logica;
  
```

Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - MDE do tipo Mealy

 

```

library ieee;
use ieee.std_logic_1164.all;

entity mde_d is
    port (ck, rst, w : in std_logic;
          z : out std_logic);
end mde_d;


architecture logica of mde_d is
    type state_type is (a, b);
    signal y : state_type;

begin
    process (rst, ck)
    begin
        if rst = '0' then
            y <= a;
        elsif (ck'event and ck = '1') then
            case y is
                when a =>
                    if w = '0' then y<=a;
                    else y<=b; end if;
                when b =>
                    if w = '0' then y<=a;
                    else y<=b; end if;
            end case;
        end if;
    end process;

    process (y, w)
    begin
        case y is
            when a => z <= '0';
            when b => z <= w;
        end case;
    end process;
end logica;
  
```


Disciplina: ELE1717 - Sistemas Digitais
Curso: Engenharia Mecatrônica

Material de suporte - Divisor de Clock

 

```
library ieee;
use ieee.std_logic_1164.all;

entity CLK_Div is
    port (clk_in : in  std_logic;
          clk_out: out std_logic);
end CLK_Div;

architecture logica of CLK_Div is
    signal ax : std_logic;
begin
    process(clk_in)
        variable cnt: integer range 0 to 13500000 := 0;
    begin
        if (rising_edge(clk_in)) then
            if (cnt=13500000) then
                cnt:=0;
                ax <= not ax;
            else
                cnt:=cnt+1;
            end if;
        end if;
        clk_out <= ax;
    end process;
end logica;
```